 


EEE 2243  
Digital System Design  
Semester II 2011/12

Quiz 1 – 2JKE1


Write the Verilog code for the following circuit:



Correct Answer:

```
module Quiz1_2JKE1_Correct(clk, In, Q);  
  
input clk, In;  
output [3:0] Q;  
reg [3:0] Q;  
  
always@(posedge clk)  
begin  
    Q[0] <= Q[3]|Q[2];  
    Q[1] <= Q[2];  
    Q[2] <= ~Q[1]&Q[0];  
    Q[3] <= In;  
end  
  
endmodule
```

RTL View:

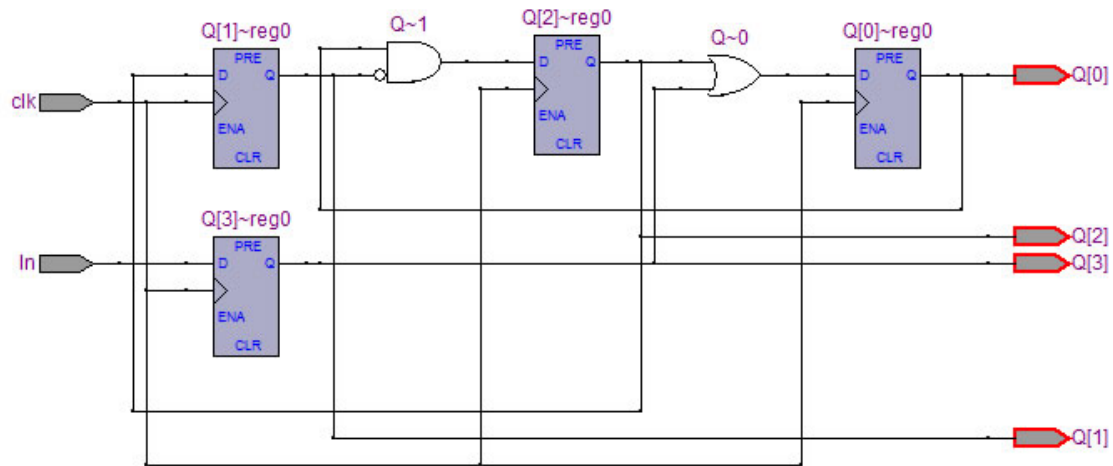

Wrong Answer:

```

module Quiz1_2JKE1_Wrong(clk, In, Q);

input clk, In;
output [3:0] Q;

assign Q[0] = Q[3]|Q[2];
assign Q[1] = Q[2];
assign Q[2] = ~Q[1]&Q[0];
assign Q[3] = In;

endmodule

```

RTL View:

