

EEE 2243
Digital System Design
Semester II 2011/12

Quiz 2 – 2JKE2

Write the Verilog code for converting D flip-flop to JK flip-flop.


Answer:

Refer to Chapter 3 slide page 26

By Boolean expression:

```
module JKFlipFlopBool(clk, J, K, Q);  
input clk, J, K;  
output Q;  
reg Q;  
  
always@(posedge clk)  
begin  
    Q <= (~K & Q) | (J & ~Q);  
end  
  
endmodule
```


RTL View:

 

By behavioral (two possible solutions):

```
module TFlipFlopBeha1(clk, J, K, Q);  
  
input clk, J, K;  
output Q;  
reg Q;  
  
always@(posedge clk)  
begin  
    if      ((J == 0) && (K == 0)) Q <= Q;  
    else if ((J == 0) && (K == 1)) Q <= 0;  
    else if ((J == 1) && (K == 0)) Q <= 1;  
    else                                     Q <= ~Q;  
end  
  
endmodule
```

RTL View:

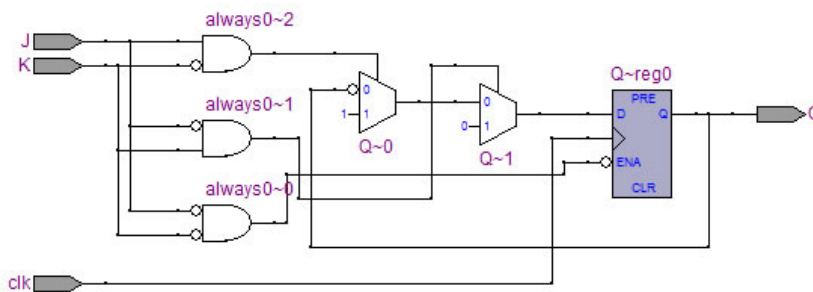

```
module TFlipFlopBeha2(clk, J, K, Q);  
  
input clk, J, K;  
output Q;  
reg Q;  
  
always@(posedge clk)  
begin  
    case ({J, K})  
        2'b00: Q <= Q;  
        2'b01: Q <= 0;  
        2'b10: Q <= 1;  
        2'b11: Q <= ~Q;  
    endcase  
end  
  
endmodule
```

RTL View:

