

EEE 2243  
Digital System Design  
Semester II 2011/12

Tutorial 1

Verilog Combinational

1. Write the Verilog code for the following 2-input Boolean gates:

a. AND gate

```
module ANDGate(A, B, F);  
input A, B;  
output F;  
  
assign F = A & B;  
  
endmodule
```

b. OR gate

```
module ORGate(A, B, F);  
input A, B;  
output F;  
  
assign F = A | B;  
  
endmodule
```

c. NOR gate

```
module NORGate(A, B, F);  
input A, B;  
output F;  
  
assign F = ~(A | B);  
  
endmodule
```

d. NAND gate

```
module NANDGate(A, B, F);  
input A, B;  
output F;  
  
assign F = ~(A & B);  
  
endmodule
```

e. XOR gate

```
module XORGate(A, B, F);  
input A, B;  
output F;  
  
assign F = A ^ B;  
  
endmodule
```

f. XNOR gate

```
module XNORGate(A, B, F);  
input A, B;  
output F;  
  
assign F = ~(A ^ B);  
  
endmodule
```

2. Write the Verilog code for the Boolean gates as in no. 1, but with 8 inputs, and forced with the following 8 bit inputs:

a. 2 dec

```
module ANDGate(F);  
output F;  
wire [7:0] inp;  
  
assign inp = 8'd2;  
  
assign F = inp[7] & inp[6] & inp[5] & inp[4] &  
inp[3] & inp[2] & inp[1] & inp[0];  
  
endmodule
```

```
module ORGate(F);  
output F;  
wire [7:0] inp;  
  
assign inp = 8'd2;  
  
assign F = inp[7] | inp[6] | inp[5] | inp[4] |  
inp[3] | inp[2] | inp[1] | inp[0];  
  
endmodule
```

```
module NORGate(F);
output F;
wire [7:0] inp;

assign inp = 8'd2;

assign F = ~(inp[7] | inp[6] | inp[5] | inp[4] |
             inp[3] | inp[2] | inp[1] | inp[0]);

endmodule
```

```
module NANDGate(F);
output F;
wire [7:0] inp;

assign inp = 8'd2;

assign F = ~(inp[7] & inp[6] & inp[5] & inp[4] &
             inp[3] & inp[2] & inp[1] & inp[0]);

endmodule
```

```
module XORGate(F);
output F;
wire [7:0] inp;

assign inp = 8'd2;

assign F = inp[7] ^ inp[6] ^ inp[5] ^ inp[4] ^
           inp[3] ^ inp[2] ^ inp[1] ^ inp[0];

endmodule
```

```
module XNORGate(F);
output F;
wire [7:0] inp;

assign inp = 8'd2;

assign F = ~(inp[7] ^ inp[6] ^ inp[5] ^ inp[4] ^
             inp[3] ^ inp[2] ^ inp[1] ^ inp[0]);

endmodule
```

b. 170 dec

```
module ANDGate(F);
output F;
wire [7:0] inp;

assign inp = 8'd170;

assign F = inp[7] & inp[6] & inp[5] & inp[4] &
           inp[3] & inp[2] & inp[1] & inp[0];

endmodule
```

```
module ORGate(F);
output F;
wire [7:0] inp;

assign inp = 8'd170;

assign F = inp[7] | inp[6] | inp[5] | inp[4] |
           inp[3] | inp[2] | inp[1] | inp[0];

endmodule
```

```
module NORGate(F);
output F;
wire [7:0] inp;

assign inp = 8'd170;

assign F = ~(inp[7] | inp[6] | inp[5] | inp[4] |
             inp[3] | inp[2] | inp[1] | inp[0]);

endmodule
```

```
module NANDGate(F);
output F;
wire [7:0] inp;

assign inp = 8'd170;

assign F = ~(inp[7] & inp[6] & inp[5] & inp[4] &
             inp[3] & inp[2] & inp[1] & inp[0]);

endmodule
```

```

module XORGate(F);
output F;
wire [7:0] inp;

assign inp = 8'd170;

assign F = inp[7] ^ inp[6] ^ inp[5] ^ inp[4] ^
           inp[3] ^ inp[2] ^ inp[1] ^ inp[0];

endmodule

```

```

module XNORGate(F);
output F;
wire [7:0] inp;

assign inp = 8'd170;

assign F = ~(inp[7] ^ inp[6] ^ inp[5] ^ inp[4] ^
             inp[3] ^ inp[2] ^ inp[1] ^ inp[0]);

endmodule

```

c. F0 hex

```

module ANDGate(F);
output F;
wire [7:0] inp;

assign inp = 8'hF0;

assign F = inp[7] & inp[6] & inp[5] & inp[4] &
           inp[3] & inp[2] & inp[1] & inp[0];

endmodule

```

```

module ORGate(F);
output F;
wire [7:0] inp;

assign inp = 8'hF0;

assign F = inp[7] | inp[6] | inp[5] | inp[4] |
           inp[3] | inp[2] | inp[1] | inp[0];

endmodule

```

```
module NORGate(F);
output F;
wire [7:0] inp;

assign inp = 8'hF0;

assign F = ~(inp[7] | inp[6] | inp[5] | inp[4] |
             inp[3] | inp[2] | inp[1] | inp[0]);

endmodule
```

```
module NANDGate(F);
output F;
wire [7:0] inp;

assign inp = 8'hF0;

assign F = ~(inp[7] & inp[6] & inp[5] & inp[4] &
             inp[3] & inp[2] & inp[1] & inp[0]);

endmodule
```

```
module XORGate(F);
output F;
wire [7:0] inp;

assign inp = 8'hF0;

assign F = inp[7] ^ inp[6] ^ inp[5] ^ inp[4] ^
           inp[3] ^ inp[2] ^ inp[1] ^ inp[0];

endmodule
```

```
module XNORGate(F);
output F;
wire [7:0] inp;

assign inp = 8'hF0;

assign F = ~(inp[7] ^ inp[6] ^ inp[5] ^ inp[4] ^
             inp[3] ^ inp[2] ^ inp[1] ^ inp[0]);

endmodule
```

d. 55 hex

```
module ANDGate(F);
output F;
wire [7:0] inp;

assign inp = 8'h55;

assign F = inp[7] & inp[6] & inp[5] & inp[4] &
           inp[3] & inp[2] & inp[1] & inp[0];

endmodule
```

```
module ORGate(F);
output F;
wire [7:0] inp;

assign inp = 8'h55;

assign F = inp[7] | inp[6] | inp[5] | inp[4] |
           inp[3] | inp[2] | inp[1] | inp[0];

endmodule
```

```
module NORGate(F);
output F;
wire [7:0] inp;

assign inp = 8'h55;

assign F = ~(inp[7] | inp[6] | inp[5] | inp[4] |
             inp[3] | inp[2] | inp[1] | inp[0]);

endmodule
```

```
module NANDGate(F);
output F;
wire [7:0] inp;

assign inp = 8'h55;

assign F = ~(inp[7] & inp[6] & inp[5] & inp[4] &
             inp[3] & inp[2] & inp[1] & inp[0]);

endmodule
```

```

module XORGate(F);
output F;
wire [7:0] inp;

assign inp = 8'h55;

assign F = inp[7] ^ inp[6] ^ inp[5] ^ inp[4] ^
           inp[3] ^ inp[2] ^ inp[1] ^ inp[0];

endmodule

```

```

module XNORGate(F);
output F;
wire [7:0] inp;

assign inp = 8'h55;

assign F = ~(inp[7] ^ inp[6] ^ inp[5] ^ inp[4] ^
             inp[3] ^ inp[2] ^ inp[1] ^ inp[0]);

endmodule

```

Which gate(s) is (are) good to tell whether the input has even number of 1-s and 0-s?

**[This information is graduate (master) level answer. It is okay if you don't know, but if you do, it will be really good.]** If we simulate the above code with enough no. values of `inp`, we can tell that, if the no. inputs is even, the XOR gate gives 1 if the no. 1-s at the inputs is odd, otherwise 0 if the no. 1-s at the inputs is even. If the no. inputs is odd, XNOR and XOR are the same.

3. Write the Verilog code for the following Boolean functions WITHOUT minimization:

a.  $f_1 = \sum m(0,2,4,5,6,7,8,10,11,12,14,15)$

```

0      ⇨      00002
2      ⇨      00102
4      ⇨      01002
5      ⇨      01012
6      ⇨      01102
7      ⇨      01112
8      ⇨      10002
10     ⇨      10102
11     ⇨      10112
12     ⇨      11002
14     ⇨      11102
15     ⇨      11112

```

```

module Q3a(a, b, c, d, f1);

input a, b, c, d;
output f1;

assign f1 =  ( ~a & ~b & ~c & ~d)
             | ( ~a & ~b &  c & ~d)
             | ( ~a &  b & ~c & ~d)
             | ( ~a &  b & ~c &  d)
             | ( ~a &  b &  c & ~d)
             | ( ~a &  b &  c &  d)
             | (  a & ~b & ~c & ~d)
             | (  a & ~b &  c & ~d)
             | (  a & ~b &  c &  d)
             | (  a &  b & ~c & ~d)
             | (  a &  b &  c & ~d)
             | (  a &  b &  c &  d);

endmodule

```

b.  $f_2 = \sum m(1,3,4,5,10,12,13)$

```

1      ⇨      00012
3      ⇨      00112
4      ⇨      01002
5      ⇨      01012
10     ⇨      10102
12     ⇨      11002
13     ⇨      11012

module Q3b(a, b, c, d, f1);

input a, b, c, d;
output f1;

assign f1 =  ( ~a & ~b & ~c &  d)
             | ( ~a & ~b &  c &  d)
             | ( ~a &  b & ~c & ~d)
             | ( ~a &  b & ~c &  d)
             | (  a & ~b &  c & ~d)
             | (  a &  b & ~c & ~d)
             | (  a &  b & ~c &  d);

endmodule

```

c.  $f_3 = \sum m(0,2,3,5,6,7,8,10,11,14,15)$

```

0      ⇨      00002
2      ⇨      00102
3      ⇨      00112
5      ⇨      01012
6      ⇨      01102
7      ⇨      01112
8      ⇨      10002
10     ⇨      10102
11     ⇨      10112
14     ⇨      11102
15     ⇨      11112

module Q3c(a, b, c, d, f1);

input a, b, c, d;
output f1;

assign f1 =  (~a & ~b & ~c & ~d)
             | (~a & ~b & c & ~d)
             | (~a & ~b & c & d)
             | (~a & b & ~c & d)
             | (~a & b & c & ~d)
             | (~a & b & c & d)
             | ( a & ~b & ~c & ~d)
             | ( a & ~b & c & ~d)
             | ( a & ~b & c & d)
             | ( a & b & c & ~d)
             | ( a & b & c & d);

endmodule

```

4. Redo number 3 using the minimized version of the functions, then compare the simulation – they should be identical.

ab cd		00	01	11	10
		00	01	11	10
cd	00	1	1	1	1
	01		1		
	11		1	1	1
	10	1	1	1	1


$$f_1 = \overline{ab} + \overline{d} + ac$$

```


module Q3a2(a, b, c, d, f1);
input a, b, c, d;
output f1;
assign f1 = (~a & b) | ~d | (a & c);
endmodule

```

Simulation of unminimized Q3a:

 

Simulation of minimized Q3a:

 

		ab			
		00	01	11	10
cd	00		1	1	
	01	1	1	1	
	11	1			
	10				1

$$f_1 = \overline{a}bd + bc + a\overline{b}c\overline{d}$$

```


module Q3b2(a, b, c, d, f1);
input a, b, c, d;
output f1;

assign f1 = (b & ~c)
            | (~a & ~b & d)
            | (a & ~b & c & ~d);


endmodule


```

Simulation of unminimized Q3b:

 

Simulation of minimized Q3b:

 

 

$$f_1 = c + \overline{bd} + \overline{abd}$$

```


module Q3c2(a, b, c, d, f1);
input a, b, c, d;
output f1;

assign f1 = c | (~b & ~d) | (~a & b & d);


endmodule

```

Simulation of unminimized Q3c:

 

Simulation of minimized Q3c:

 

5. Write Verilog code for the circuit in Figure Q5 with and without wires. Compare the RTL view and simulation.

 


Figure Q5



Without wire:

```

module Q5i(A, B, C, D, F);
input A, B, C, D;
output F;



assign F = ((B|C)&A)|~(~A&D);
endmodule

```

  

With wire:

```
module Q5ii(A, B, C, D, F);  
  input A, B, C, D;  
  output F;  
  wire W1, W2, W3;  
  
  assign W1 = B | C;  
  assign W2 = W1 & A;  
  assign W3 = ~(~A & D);  
  assign F = W2 | W3;  
  
endmodule
```

  


6. Write Verilog code for a tri-state buffer and another one for a tri-state inverter.


```
Tri-state buffer:
module TriStateBuffer(Lin, Lout, EN);
input Lin, EN;
output Lout;
reg Lout;

always@(Lin or EN)
begin
    if (EN)
        Lout <= Lin;
    else
        Lout <= 1'bz;
end
endmodule
```

RTL View:

 


Simulation:

 

```
Tri-state buffer:
module TriStateInverter(Lin, Lout, EN);
input Lin, EN;
output Lout;
reg Lout;

always@(Lin or EN)
begin
    if (EN)
        Lout <= ~Lin;
    else
        Lout <= 1'bz;
end
endmodule
```

RTL View:

 

Simulation:

