

EEE 2243
Digital System Design
Semester II 2011/12

Tutorial 2


Verilog Sequential

1. Write the Verilog code for the following counters by behavioral approach:

a. $5 \rightarrow 7 \rightarrow 9 \rightarrow 11 \rightarrow 13$ repeat


```
module Counter1a(clk, ctr);  
  
input clk;  
output [3:0] ctr;  
reg [3:0] ctr;  
  
initial ctr <= 5;  
  
always@(posedge clk)  
begin  
    if (ctr == 13)  
        ctr <= 5;  
    else  
        ctr <= ctr+2;  
    end  
end  
  
endmodule
```

Simulation:

 

 
b. $9 \rightarrow 7 \rightarrow 8 \rightarrow 5 \rightarrow 1$ repeat

```
module Counter1b(clk, ctr);  
  
    input clk;  
    output [3:0] ctr;  
    reg [3:0] ctr;  
  
    initial ctr <= 9;  
  
    always@(posedge clk)  
    case (ctr)  
        9: ctr <= 7;  
        7: ctr <= 8;  
        8: ctr <= 5;  
        5: ctr <= 1;  
        1: ctr <= 9;  
    endcase  
  
endmodule  
  
Simulation:
```



 c. 4 bit mod 6 start at 12

```
module Counter1c(clk, ctr);  
  
    input clk;  
    output [3:0] ctr;  
    reg [3:0] ctr;  
  
    initial ctr <= 12;  
  
    always@(posedge clk)  
    if (ctr == 2)  
        ctr <= 12;  
    else  
        ctr <= ctr+1;  
    endmodule  
  
Simulation:
```



- d. 4 bit mod 6 start at 13 increment by 2

```
module Counter1d(clk, ctr);  
    input clk;  
    output [3:0] ctr;  
    reg [3:0] ctr;  
  
    initial ctr <= 13;  
  
    always@(posedge clk)  
        if (ctr == 7)  
            ctr <= 13;  
        else  
            ctr <= ctr+2;  
  
endmodule  
  
Simulation:
```



- e. $9 \rightarrow 7 \rightarrow 8 \rightarrow 5 \rightarrow 1 \rightarrow 3 \rightarrow 4 \rightarrow 5$ repeat [This might be a difficult one]

This question might be misleading. The values that are written in the state transition list above are supposed to be the output of the FSM at each state, not the state value itself. In this case the first output 5 and the second output 5 are not from the same state; only the the output is the same which is 5. The total number of states is then 8 that we can number consecutively. The output assignment then can be set separately.


```
module Counter1e(clk, ctr);  
    input clk;  
    output [3:0] ctr;  
    reg [3:0] ctr;  
    reg [2:0] state;  
  
    initial  
    begin  
        state <= 0;  
        ctr <= 9;  
    end  
  
end
```

```

always@(posedge clk)
begin
    state <= state+1;
    case (state)
        0: ctr <= 9;
        1: ctr <= 7;
        2: ctr <= 8;
        3: ctr <= 5;
        4: ctr <= 1;
        5: ctr <= 3;
        6: ctr <= 4;
        7: ctr <= 5;
    endcase
end
endmodule

```

Simulation:

 

Simulate each and every one of them.

- Write the Verilog code for 8 bit Johnson and ring counter using Boolean expression and behavioral approach.

```

module JohnsonBoolean(clk, state);

input clk;
output [7:0] state;
reg [7:0] state;

initial state <= 0;

always@(posedge clk)
begin
    state[0] <= state[1];
    state[1] <= state[2];
    state[2] <= state[3];
    state[3] <= state[4];
    state[4] <= state[5];
    state[5] <= state[6];
    state[6] <= state[7];
    state[7] <= ~state[0];
end

endmodule

```

```

module JohnsonBehavioral(clk, state);

input clk;
output [7:0] state;
reg [7:0] state;

initial state <= 0;

always@(posedge clk)
begin
    case (state)
        4'b00000000: state <= 4'b10000000;
        4'b10000000: state <= 4'b11000000;
        4'b11000000: state <= 4'b11100000;
        4'b11100000: state <= 4'b11110000;
        4'b11110000: state <= 4'b11111000;
        4'b11111000: state <= 4'b11111100;
        4'b11111100: state <= 4'b11111110;
        4'b11111110: state <= 4'b11111111;
        4'b11111111: state <= 4'b01111111;
        4'b01111111: state <= 4'b00111111;
        4'b00111111: state <= 4'b00011111;
        4'b00011111: state <= 4'b00001111;
        4'b00001111: state <= 4'b00000111;
        4'b00000111: state <= 4'b00000011;
        4'b00000011: state <= 4'b00000001;
        4'b00000001: state <= 4'b00000000;
    endcase
end

```

```

module RingBoolean(clk, state);

input clk;
output [3:0] state;
reg [3:0] state;

initial state <= 4'b10000000;

always@(posedge clk)
begin
    state[0] <= state[1];
    state[1] <= state[2];
    state[2] <= state[3];
    state[3] <= state[4];
    state[4] <= state[5];
    state[5] <= state[6];
    state[6] <= state[7];
    state[7] <= state[0];
end

endmodule

```

```

module RingBehavioral(clk, state);

input clk;
output [3:0] state;
reg [3:0] state;

initial state <= 4'b10000000;

always@(posedge clk)
begin
    case (state)
        4'b10000000: state <= 4'b01000000;
        4'b01000000: state <= 4'b00100000;
        4'b00100000: state <= 4'b00010000;
        4'b00010000: state <= 4'b00001000;
        4'b00001000: state <= 4'b00000100;
        4'b00000100: state <= 4'b00000010;
        4'b00000010: state <= 4'b00000001;
        4'b00000001: state <= 4'b10000000;
    endcase
end

endmodule


```

3. Let's design a state-machine-based controller using a similar (but not exactly the same) approach as given by Vahid in Chapter 2 slide's page 22. The OUTPUT transition is:


11110000 → 00111100 → 10100101 → 01011010 repeat

[This is an exercise to test whether you can follow instruction or not.]

 - i. Assign each output to a state and draw the state diagram.



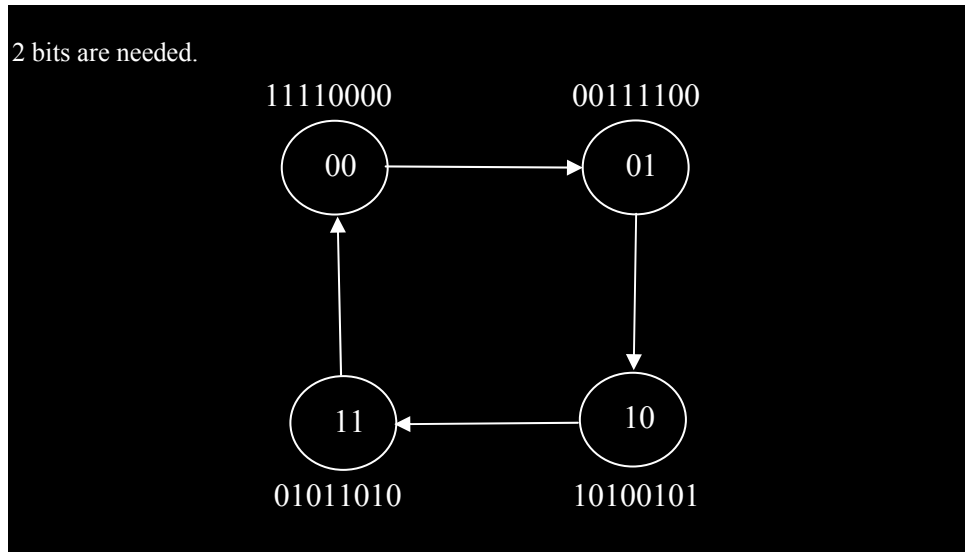- ii. Assign each state with a binary value. How many bits do you need?



- iii. Construct an excitation table (truth table for sequential circuit) to show the state transition.

Current State	Next State
00	01
01	10
10	11
11	00

- iv. Construct a truth table to show which state produces which output pattern.

State	Output
00	11110000
01	00111100
10	10100101
11	01011010

- v. Write the Verilog code to implement the excitation table in (iii).

```

module StepperMotor(clk, Op);

input clk;
output [7:0] Op;
reg [7:0] Op;
reg [1:0] state;

initial state <= 2'b00;

always@(posedge clk)
begin
    case (state)
        2'b00: state <= 2'b01;
        2'b01: state <= 2'b10;
        2'b10: state <= 2'b11;
        2'b11: state <= 2'b00;
    endcase
end

endmodule

```

- vi. In the same code, implement the Boolean expression to compute the output from the state as input.

```

module StepperMotor(clk, Op);

input clk;
output [7:0] Op;
reg [7:0] Op;
reg [1:0] state;

initial
begin
    state <= 2'b00;
    Op <= 8'b111110000;
end

always@(posedge clk)
begin
    case (state)
        2'b00: state = 2'b01;
        2'b01: state = 2'b10;
        2'b10: state = 2'b11;
        2'b11: state = 2'b00;
    endcase
    if (state == 2'b00) Op = 8'b111110000;
    else if (state == 2'b01) Op = 8'b001111100;
    else if (state == 2'b10) Op = 8'b10101010;
    else Op = 8'b010111010;
end


endmodule

```


- vii. Re-write the whole code using pure behavioral approach. The output simulation waveforms must be the same for the two implementations, but compare the RTL views and try to explain the differences.

```
module StepperMotor2(clk, Op);  
  
input clk;  
output [7:0] Op;  
reg [7:0] Op;  
  
initial Op <= 8'b11110000;  
  
always@(posedge clk)  
begin  
    case (Op)  
        8'b11110000: Op <= 8'b00111100;  
        8'b00111100: Op <= 8'b10100101;  
        8'b10100101: Op <= 8'b01011010;  
        8'b01011010: Op <= 8'b11110000;  
    endcase  
end  
  
endmodule
```


Simulation of StepperMotor:

 

Simulation of StepperMotor2:

 

RTL View of StepperMotor:

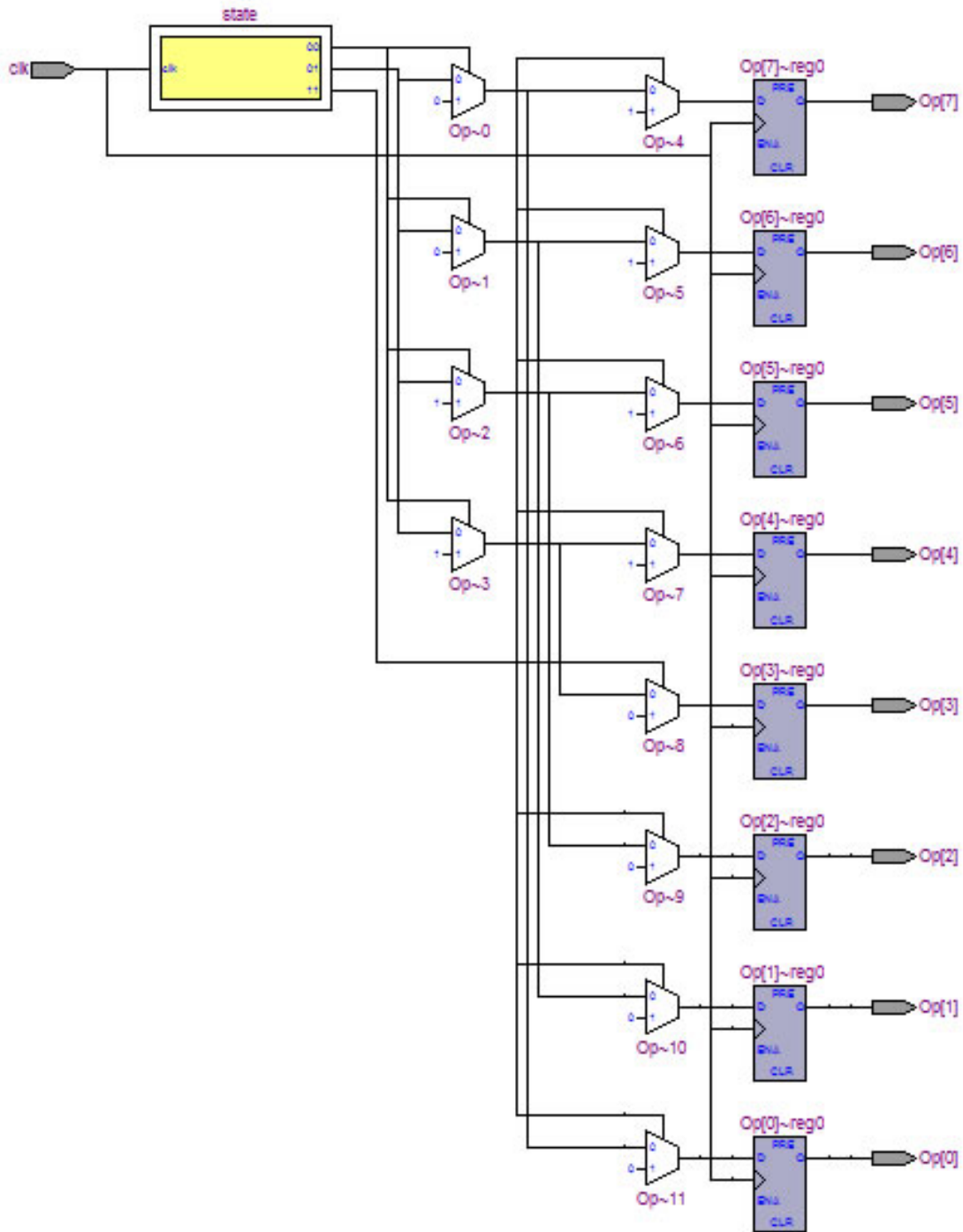

RTL View of StepperMotor2 is too complicated to be posted in this document. This clearly shows that, while it requires more coding, Vahid's approach results in better circuit. The state machine (yellow box) in the approach has reduced many of the complications.

4. Using the 3 bit shift register given in Figure Q4, construct a sequential system that is capable of detecting an input sequence of 101, i.e. it gives an output 1 after it receives 101.


 


Figure Q4

 

5. Using the same 3 bit shift register as in Question 5, construct a sequential system that is capable of detecting a sequence of binary pattern that contains only one bit 1 stored in the register.

