

EEE 2243
Digital System Design
Semester II 2011/12

Tutorial 3


Verilog of Elementary Components

1. Write the Verilog code for the following decoders in Boolean expression approach:

a. 2-to-4 active high

```
module Decoder_2_4_H(Lin, Lout);  
  
input [1:0] Lin;  
output [3:0] Lout;  
  
assign Lout[0] = ~Lin[1] & ~Lin[0];  
assign Lout[1] = ~Lin[1] & Lin[0];  
assign Lout[2] = Lin[1] & ~Lin[0];  
assign Lout[3] = Lin[1] & Lin[0];  
  
endmodule
```


Simulation:

 

b. 2-to-4 active low

```
module Decoder_2_4_L(Lin, Lout);  
  
input [1:0] Lin;  
output [3:0] Lout;  
  
assign Lout[0] = ~(~Lin[1] & ~Lin[0]);  
assign Lout[1] = ~(~Lin[1] & Lin[0]);  
assign Lout[2] = ~(Lin[1] & ~Lin[0]);  
assign Lout[3] = ~(Lin[1] & Lin[0]);  
  
endmodule
```

Simulation:

 

c. 3-to-8 active high

```
module Decoder_3_8_H(Lin, Lout);  
  
    input [2:0] Lin;  
    output [7:0] Lout;  
  
    assign Lout[0] = ~Lin[2] & ~Lin[1] & ~Lin[0];  
    assign Lout[1] = ~Lin[2] & ~Lin[1] & Lin[0];  
    assign Lout[2] = ~Lin[2] & Lin[1] & ~Lin[0];  
    assign Lout[3] = ~Lin[2] & Lin[1] & Lin[0];  
    assign Lout[4] = Lin[2] & ~Lin[1] & ~Lin[0];  
    assign Lout[5] = Lin[2] & ~Lin[1] & Lin[0];  
    assign Lout[6] = Lin[2] & Lin[1] & ~Lin[0];  
    assign Lout[7] = Lin[2] & Lin[1] & Lin[0];  
  
endmodule
```

d. 3-to-8 active low

```
module Decoder_3_8_L(Lin, Lout);  
  
    input [2:0] Lin;  
    output [7:0] Lout;  
  
    assign Lout[0] = ~(~Lin[2] & ~Lin[1] & ~Lin[0]);  
    assign Lout[1] = ~(~Lin[2] & ~Lin[1] & Lin[0]);  
    assign Lout[2] = ~(~Lin[2] & Lin[1] & ~Lin[0]);  
    assign Lout[3] = ~(~Lin[2] & Lin[1] & Lin[0]);  
    assign Lout[4] = ~(Lin[2] & ~Lin[1] & ~Lin[0]);  
    assign Lout[5] = ~(Lin[2] & ~Lin[1] & Lin[0]);  
    assign Lout[6] = ~(Lin[2] & Lin[1] & ~Lin[0]);  
    assign Lout[7] = ~(Lin[2] & Lin[1] & Lin[0]);  
  
endmodule
```

Simulate the 2-to-4 decoders.

2. Write the Verilog code for 4-to-1 and 8-to-1 multiplexers in Boolean expression and behavioral approach.

For Boolean approach follow the circuit in slide for chapter 3 page 14.

```
module Mux4Bool(Lin, Sel, Lout);  
  
input [3:0] Lin;  
input [1:0] Sel;  
output Lout;  
  
assign Lout = (~Sel[1] & ~Sel[0] & Lin[0]) |  
              (~Sel[1] & Sel[0] & Lin[1]) |  
              ( Sel[1] & ~Sel[0] & Lin[2]) |  
              ( Sel[1] & Sel[0] & Lin[3]);  
  
endmodule
```

```
module Mux8Bool(Lin, Sel, Lout);  
  
input [7:0] Lin;  
input [2:0] Sel;  
output Lout;  
  
assign Lout = (~Sel[2] & ~Sel[1] & ~Sel[0] & Lin[0]) |  
              (~Sel[2] & ~Sel[1] & Sel[0] & Lin[1]) |  
              (~Sel[2] & Sel[1] & ~Sel[0] & Lin[2]) |  
              (~Sel[2] & Sel[1] & Sel[0] & Lin[3]) |  
              ( Sel[2] & ~Sel[1] & ~Sel[0] & Lin[4]) |  
              ( Sel[2] & ~Sel[1] & Sel[0] & Lin[5]) |  
              ( Sel[2] & Sel[1] & ~Sel[0] & Lin[6]) |  
              ( Sel[2] & Sel[1] & Sel[0] & Lin[7]);  
  
endmodule
```

```
module Mux4Beha(Lin, Sel, Lout);  
  
input [3:0] Lin;  
input [1:0] Sel;  
output Lout;  
reg Lout  
  
always@(*)  
begin  
    case (Sel)  
        0: Lout <= Lin[0];  
        1: Lout <= Lin[1];  
        2: Lout <= Lin[2];  
        3: Lout <= Lin[3];  
    endcase  
end  
  
endmodule
```

```

module Mux8Beha(Lin, Sel, Lout);

input [7:0] Lin;
input [2:0] Sel;
output Lout;

always@(*)
begin
    case (Sel)
        0: Lout <= Lin[0];
        1: Lout <= Lin[1];
        2: Lout <= Lin[2];
        3: Lout <= Lin[3];
        4: Lout <= Lin[4];
        5: Lout <= Lin[5];
        6: Lout <= Lin[6];
        7: Lout <= Lin[7];
    endcase
end
endmodule

```

3. Repeat no. 2 but now add another input called “active low output enable.” It means the output has effect only if that input is LOW, otherwise the output will be a high-Z. Simulate at least one of them.

```


module Mux4Bool(Lin, Sel, Lout, EN);

input EN;
input [3:0] Lin;
input [1:0] Sel;
output Lout;

assign Lout = (EN) ?
    1'bz :
    ((~Sel[1] & ~Sel[0] & Lin[0]) |
     (~Sel[1] & Sel[0] & Lin[1]) |
     ( Sel[1] & ~Sel[0] & Lin[2]) |
     ( Sel[1] & Sel[0] & Lin[3]));

endmodule

```

 

```

module Mux8Bool(Lin, Sel, Lout);

input EN;
input [7:0] Lin;
input [2:0] Sel;
output Lout;

assign Lout = (EN) ?
    1'bz :
    ((~Sel[2] & ~Sel[1] & ~Sel[0] & Lin[0]) |
     (~Sel[2] & ~Sel[1] & Sel[0] & Lin[1]) |
     (~Sel[2] & Sel[1] & ~Sel[0] & Lin[2]) |
     (~Sel[2] & Sel[1] & Sel[0] & Lin[3]) |
     ( Sel[2] & ~Sel[1] & ~Sel[0] & Lin[4]) |
     ( Sel[2] & ~Sel[1] & Sel[0] & Lin[5]) |
     ( Sel[2] & Sel[1] & ~Sel[0] & Lin[6]) |
     ( Sel[2] & Sel[1] & Sel[0] & Lin[7]));

endmodule

```

```

module Mux4Beha(Lin, Sel, Lout);

input EN;
input [3:0] Lin;
input [1:0] Sel;
output Lout;
reg Lout;

always@(*)
begin
    case (Sel)
        0: Lout <= (EN) ? 1'bz : Lin[0];
        1: Lout <= (EN) ? 1'bz : Lin[1];
        2: Lout <= (EN) ? 1'bz : Lin[2];
        3: Lout <= (EN) ? 1'bz : Lin[3];
    endcase
end

endmodule

```

```

module Mux8Beha(Lin, Sel, Lout);

input EN;
input [7:0] Lin;
input [2:0] Sel;
output Lout;
reg Lout;

always@(*)
begin
    case (Sel)
        0: Lout <= (EN) ? 1'bz : Lin[0];
        1: Lout <= (EN) ? 1'bz : Lin[1];
        2: Lout <= (EN) ? 1'bz : Lin[2];
        3: Lout <= (EN) ? 1'bz : Lin[3];
        4: Lout <= (EN) ? 1'bz : Lin[4];
        5: Lout <= (EN) ? 1'bz : Lin[5];
        6: Lout <= (EN) ? 1'bz : Lin[6];
        7: Lout <= (EN) ? 1'bz : Lin[7];
    endcase
end

endmodule

```

4. Extend the decoders in no. 1 to their corresponding demultiplexers. Hint: It is easier to keep it as Boolean expression approach.

```

module Demux4(Lin, Lout, Sel);

input Lin;
input [1:0] Sel;
output [3:0] Lout;

assign Lout[0] = ~Sel[1] & ~Sel[0] & Lin;
assign Lout[1] = ~Sel[1] & Sel[0] & Lin;
assign Lout[2] = Sel[1] & ~Sel[0] & Lin;
assign Lout[3] = Sel[1] & Sel[0] & Lin;

endmodule

```

```

module Demux8(Lin, Lout, Sel);

input Lin;
input [2:0] Sel;
output [7:0] Lout;

assign Lout[0] = ~Sel[2] & ~Sel[1] & ~Sel[0] & Lin;
assign Lout[1] = ~Sel[2] & ~Sel[1] & Sel[0] & Lin;
assign Lout[2] = ~Sel[2] & Sel[1] & ~Sel[0] & Lin;
assign Lout[3] = ~Sel[2] & Sel[1] & Sel[0] & Lin;
assign Lout[4] = Sel[2] & ~Sel[1] & ~Sel[0] & Lin;
assign Lout[5] = Sel[2] & ~Sel[1] & Sel[0] & Lin;
assign Lout[6] = Sel[2] & Sel[1] & ~Sel[0] & Lin;
assign Lout[7] = Sel[2] & Sel[1] & Sel[0] & Lin;

endmodule

```

5. In both Boolean and behavioral approaches, write the Verilog code for converting D flip-flops into T and JK flip-flop.

```

module TFlipFlopBool(clk, T, Q);

input T, clk;
output Q;
reg Q;

always@(posedge clk)
begin
    Q <= (~T & Q) | (T & ~Q);
end

endmodule

```

```

module TFlipFlopBeha(clk, T, Q);

input T, clk;
output Q;
reg Q;

always@(posedge clk)
begin
    if (T == 1)
        Q <= ~Q;
    else
        Q <= Q;
end

endmodule

```

